

P2 – Electricity

Current, resistance and potential difference


Electrical current is the flow of electrical charge.

Current is measured in amps (A), charge is measured in Coulombs (C).

The size of the current depends on the rate of the flow of charge – ie how many coulombs of charge per second.

$$Q = I t$$

Charge = Current x time
(C) (A) (s)

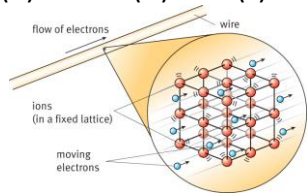

Ohms Law


The current through a component depends on the potential difference and the resistance of the component.

If a component has high resistance, the current will be smaller for a given potential difference

potential difference = current x resistance

$$V = I R$$

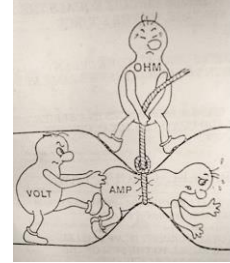
pd is measured in volts (V), resistance in Ohms (Ω)



Series and parallel circuits

Series circuits:

A series circuit is one single loop

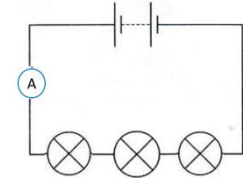


In a series circuit:

- the current is the same at all points in the circuit.
- potential difference is shared between components (equally if components are identical resistance)
- total resistance = sum of all resistors

Parallel circuits

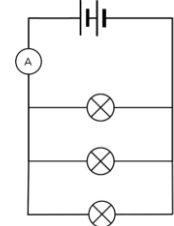A parallel circuit consists of more than one loop from the battery/cell.



In a parallel circuit:

- The current is shared amongst the branches
- The potential difference is the same across all components
- Resistance in the whole circuit is LESS than that of the smallest resistor

Hypothesis 'the length of the wire affects resistance'



Independent variable – length of wire

Dependent variable – resistance

Control variables – type of wire, temperature of the wire, diameter of the wire

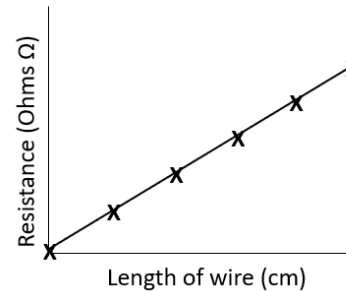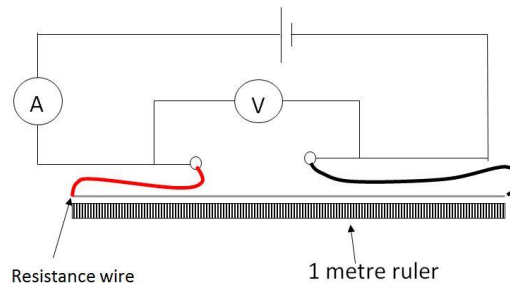1. Set up the circuit as shown, with an ammeter in the circuit and a voltmeter connected across the wire
2. Use crocodile clips to change the length of the wire in the circuit
3. Make the wire 10cm long and read the current and pd. Switch off the current between readings or the wire will get hot, increasing the resistance.
4. Repeat for 20, 30, 40, 50 cm. (5 minimum)
5. Calculate resistance using Ohms Law $R = V/I$


Plot length of wire (IV) against resistance (DV)



The relationship is directly proportional


P2 – Electricity

Components

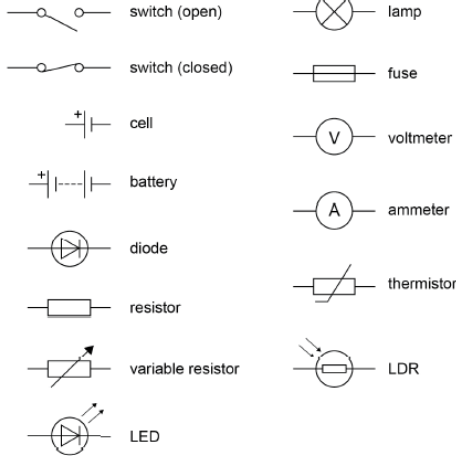


- A **diode** only allows current to flow one way in a circuit
- A **resistor** is a component that provides a fixed resistance in the circuit – e.g a 5 Ω resistor
- A **variable resistor** is a component whose resistance can be changed (e.g a dimmer switch)
- A **thermistor** is a resistor whose resistance changes with temperature – the higher the temperature the lower the resistance
- An **LDR** (light dependent resistor) has resistance that changes
- An **LED** (light emitting diode) is a light that only allows the flow of current one way


LDR

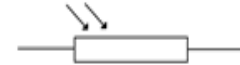

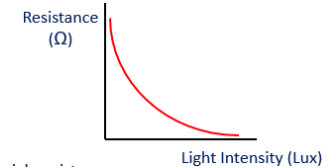A light dependent resistor has varying resistance.
As the light intensity increases, the resistance decreases



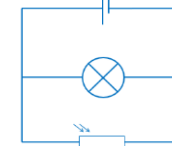LDRs can be used to switch on lights at night time.



In this circuit, when it is day time, the resistance in the LDR is low, so all current flows through the LDR.


As light levels fall, resistance increases, until eventually there is less resistance in the bulb than the LDR, so current flows through the bulb – switching it on.

Thermistor




As the temperature increases, the resistance in a thermistor decreases.

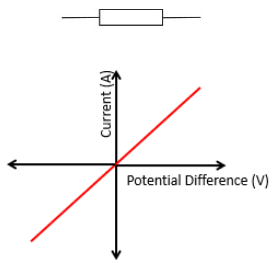
Current, potential difference and resistance for different components



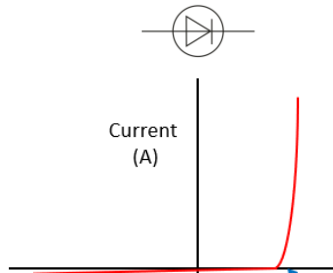A fixed (ohmic) resistor has fixed resistance
current is directly proportional to potential difference
Resistance remains constant (at constant temp)



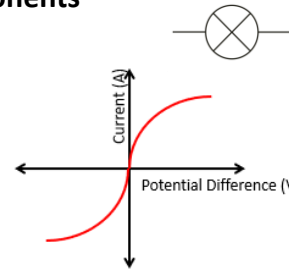A diode very high resistance in one direction.
Only when the potential difference is positive does current flow



A filament bulb contains a thin wire that glows as current flows.
As the pd increases, the current initially increases.
However, at higher pd, the wire gets hot
The ions in the wire move faster and collide with the moving charges
Resistance increases, so current stops increasing

P2 – Electricity

Domestic use of electricity

There are two types of electrical supply – direct (DC) and alternating current (AC)



AC

The pd changes direction and magnitude, giving alternating current

The number of times the change of direction happens per second is the frequency.

UK mains is AC - **230V**


Frequency of **50 Hz**

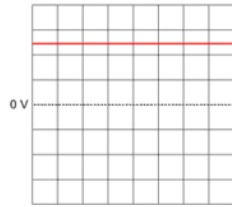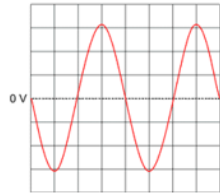

DC

A direct pd produces current that flows in one direction

Batteries supply DC

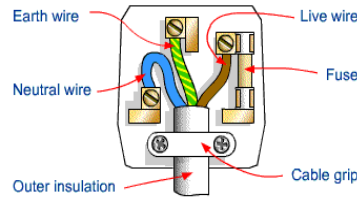

Electrical appliances are connected using 3 core cable

- Brown – live wire, with pd of 230V
- Blue – neutral, 0V, completes the circuit
- Yellow and green – Earth wire, is at 0V unless there is a fault, when it will become live

Appliances in the home and power

Power is measured in Watts (W) or kW

Power can be calculated by using:

Power = Voltage x current

$$P = IV$$

Power = current² x resistance

$$P = I^2 R$$

Appliances transfer energy.

Energy is measured in Joules (J) or kJ

The energy transferred can be calculated by using:

Energy = charge flow x potential difference

$$E = QV$$

Energy = power x time

$$E = p t$$


For example

A kettle transfers energy from the thermal store of the filament in the kettle to the thermal store of the water inside.

Some energy is transferred to the thermal store of the surroundings.

The National Grid

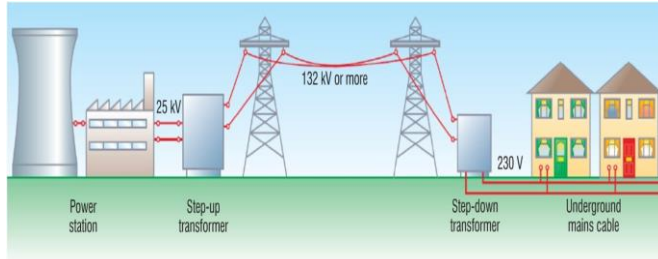The National Grid is a system of cables and transformers connecting power stations to homes and businesses



The National Grid uses very high pd and low current.

High current causes heating in the wires and would result in large energy losses.

Step up transformers increase the pd from the power station (to around 400000V) so that low current can be used to transmit power.

This means the wires don't get hot, so less energy is lost.

Near homes and businesses, step down transformers reduce the pd to 230V for safety.